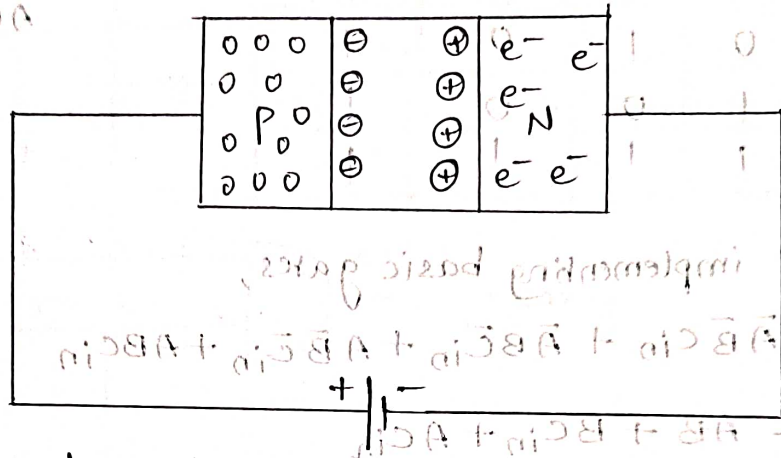


# ASSIGNMENT - 1B


1) Explain forward and reverse bias of semiconductor diode with V-I characteristics.

→ \* Forward Bias

° PN junction said to be forward bias when the positive terminal of the battery is connected to P-type and negative terminal of the battery is connected to n-type as shown in the figure.



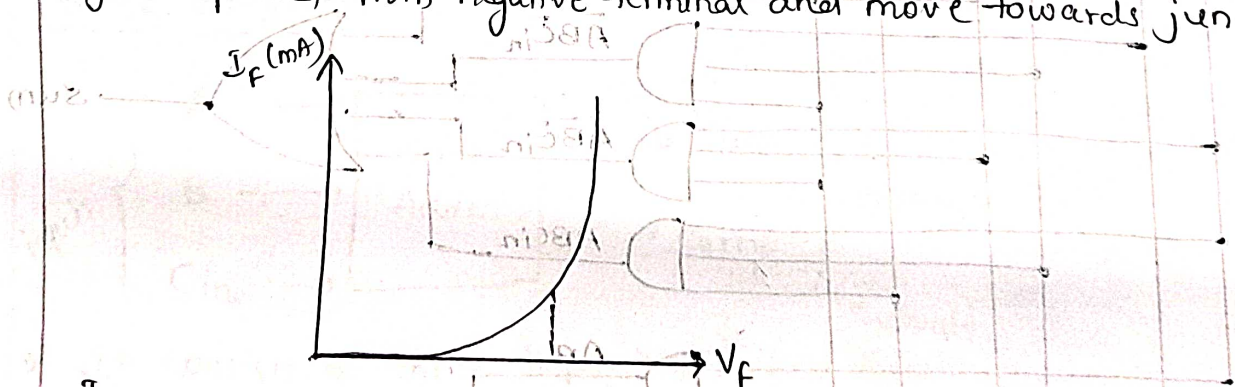
- If the applied voltage is less than the barrier potential there will be no conduction.
- When the applied voltage is more than the barrier potential then the holes on p-side which are positively charged gets repelled from positive terminal and driven towards junction.
- Similarly the electrons on n-side which are negatively charged gets repelled from negative terminal and move towards junction.



In case of forward bias the circuit will be act as a close and hence current is maximum and voltage is equal to zero.


\* reverse bias

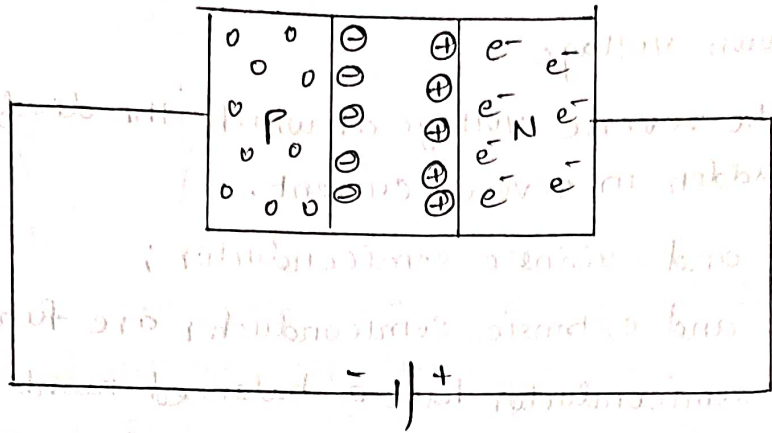- PN junction is said to reverse biased when the positive terminal of battery is connected to n-type & negative terminal of battery is connected to p-type.



- When p-n junction is reverse biased then the holes on p-side of junction acts attracted towards negative terminals and electrons on junction are attracted positive terminal of the battery.
- Thus holes on pside and electrons on n-side move away from the junction thereby increase the barrier potential.
- If the barrier voltage is increased, majority charged carrier cannot occurs the junction and there is no current flow across junction.
- Minority charge carriers cross the junction and leads to a small current flow called reverse current as shown in figure.

V-I characteristics

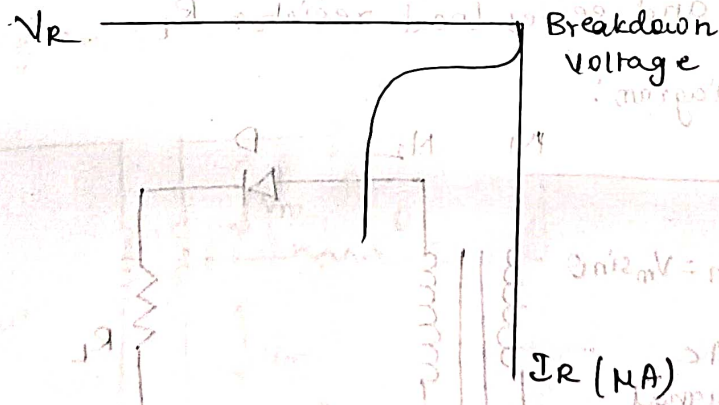

In case of reverse bias the circuit will be acts as open circuit hence current is equal to zero and voltage is equal to maximum.

2) Write a short note on

a) knee voltage:

→ It is the forward voltage at which the diode starts conducting.

b) Breakdown voltage

→ It is the reverse voltage at which the diode break down with sudden in reverse current.

c) intrinsic and extrinsic semiconductor;

Intrinsic and extrinsic semiconductor are fundamental.

Intrinsic semiconductor have a balanced number of electrons

and holes while extrinsic semiconductor have impurities

semi-conductor can be either n-type or p-type.

5) Explain with a neat circuit diagram and waveform,


a) Half wave rectifier.

→ Rectifier which conducts current or voltage only during one half cycle of AC input is called half wave rectifier.


• Figure shows full wave rectifier which single diode acts as half wave rectifier.

• AC input supply to be rectified is supplied through transformer to diodes and series load resistor  $R_L$

Circuit diagram:

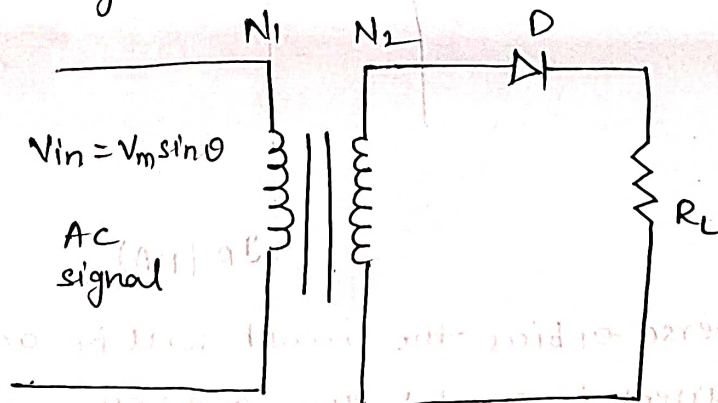

Waveform:

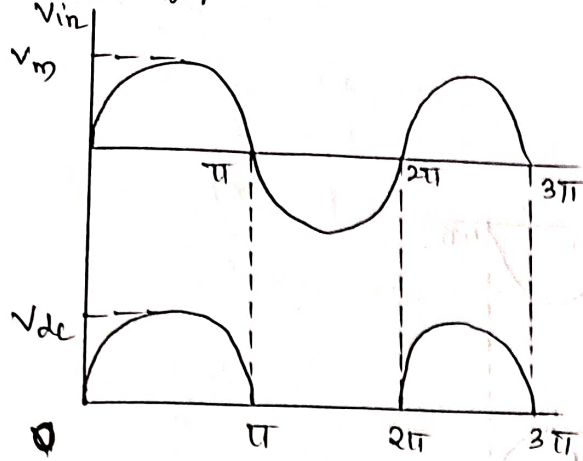


- During positive half cycle of supply voltage - diode is said to be forward biased acts as short circuit and current flows through  $R_L$  therefore  $V_o = +V_{in}$
- During negative half cycle of supply diode is said to be reverse biased acts as open circuit and current do not flows through  $R_L$  therefore  $V_o = 0$ .


b) full wave rectifier:

- full wave rectifier converts both half cycle of AC input signal to pulsating dc.
- It consists of two diodes as shown in figure.
- Centre tapping in the secondary of the waveform is done to obtain two equal voltage but opposite phase.

circuit diagram:

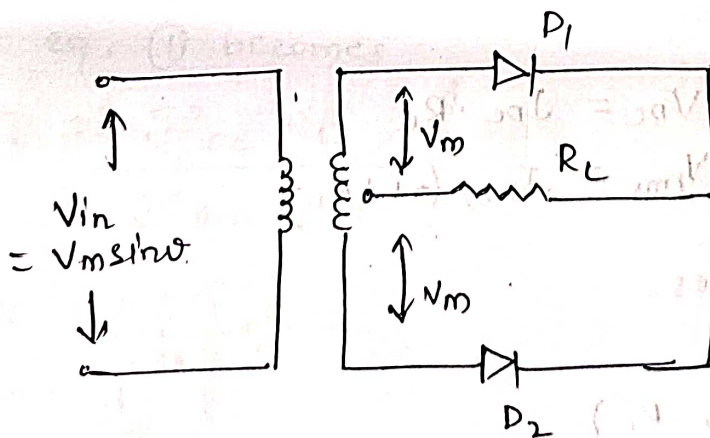

waveform :

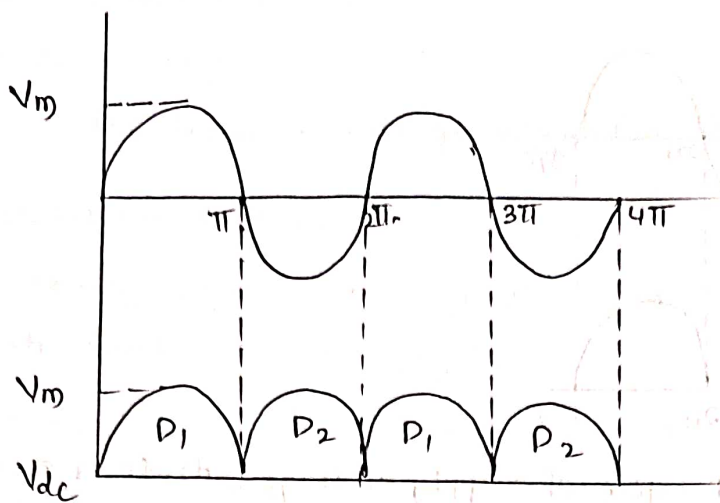

- During positive half cycle,  $D_1$  is conducting and  $D_2$  is not conducting.
- During negative half cycle,  $D_1$  is non-conducting and  $D_2$  is conducting.
- In this way, a full wave rectifier converts both negative and positive half cycles of AC input to DC output.

6) Derive the expression of efficiency for  
a) Half wave rectifier ;

→ Efficiency  $\Rightarrow \eta = \frac{\text{output power}}{\text{input power}} = \frac{P_{DC}}{P_{AC}}$

$$\eta = \frac{V_{DC} \cdot I_{DC}}{V_{RMS} \cdot I_{RMS}} \quad \text{--- (1)}$$

for HWR, let  $V_{DC} = I_{DC} \cdot R_L$   
 $V_{RMS} = I_{RMS} (\tau_f + R_L)$

$\therefore$  eq, (1) becomes.

$$\eta = \frac{I_{DC} (I_{DC} \cdot R_L)}{I_{RMS} (I_{RMS} (\tau_f + R_L))}$$

$$\eta = \frac{I_{DC}^2 R_L}{I_{RMS}^2 (R_L + r_F)}$$

$$I_{DC} = \frac{I_m}{\pi}$$

$$I_{RMS} = \frac{I_m}{2}$$

$$\eta = \frac{I_{DC}^2 R_L}{I_{RMS}^2 (R_L + r_F)} \times \frac{1}{1}$$

$$R_L \gg r_F$$

$$\eta = \frac{\left(\frac{I_m}{\pi}\right)^2}{\left(\frac{I_m}{2}\right)^2} = \frac{I_m^2}{\pi^2} \times \frac{4}{I_m^2} = \frac{4}{\pi^2}$$

$$\therefore \eta = \frac{4}{\pi^2} \times 100 = 0.405 \times 100 = 40.5$$

$$\boxed{\therefore \eta = 40.5\%}$$

b) Full wave rectifier (Centre tap)

$$\rightarrow \text{Efficiency} \Rightarrow \eta = \frac{P_{\text{output}}}{P_{\text{input}}} = \frac{P_{DC}}{P_{AC}}$$

$$\eta = \frac{V_{DC} \cdot I_{DC}}{V_{RMS} \cdot I_{RMS}} \quad \text{--- (1)}$$

$$\text{Let } V_{DC} = I_{DC} \times R_L \quad V_{RMS} = I_{RMS} \times (r_F + R_L)$$

\(\therefore\) eq. (1) becomes

$$\because R_L \gg r_F$$

$$\eta = \frac{I_{DC}^2 R_L}{I_{RMS}^2 (R_L + r_F)} \times \frac{1}{1}$$

$$I_{DC} = \frac{2I_m}{\pi}$$

$$I_{RMS} = \frac{I_m}{\sqrt{2}}$$

$$= \frac{2I_m^2}{\pi^2} \times \frac{4}{I_m^2} = \frac{8}{\pi^2} \times 100 = 0.8105 \times 100$$

$$\boxed{\therefore \eta = 81.05\%}$$

3) What do you understand by a semiconductor? Discuss important properties of semi-conductor.



- o) Semiconductors are materials that have the conductivity between a conductor and an insulator. The most popular semiconductors are silicon and germanium.
- o) Semiconductors are of 2 types: Intrinsic & extrinsic semiconductors
- o) Intrinsic semiconductors are pure semi-conductors. They will not have any impurities added to it while, extrinsic semiconductors are semiconductors with impurities.

\* Properties of semi-conductors:-

1. The resistivity of semi-conductors lies between a conductor and an insulator.
2. Doping increases conductivity of semi-conductor.
3. They are formed by a covalent bonds.
4. At absolute zero temperature, it behaves as a perfect insulator.
5. At room temperature, it behaves as a conductor.
6. If we increase the temperature of semi-conductor, its electrical conductivity also increases.
7. They have small energy gap (or) band gap.


4) What is a p-n junction? Explain the formation of potential barrier in a p-n junction.




P-N junction

A p-n junction is an interface or a boundary between two semi-conductor material types, namely the p-type and the n-type, inside a semi-conductor.

- A p-n junction is formed by bringing p-type & n-type semi-conductors together in very close proximity.
- At the instant of p-n junction, movement of free electrons from the n-side and free holes from the p-side diffuse across the junction and combine and thus leave -ve ions on the p-side and +ve ions in n-side.
- These two layers of +ve & -ve ions form the depletion region and the potential difference thus sets up is called as potential barrier.

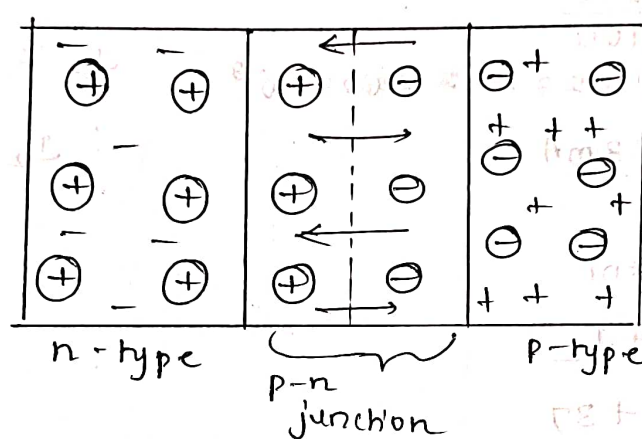

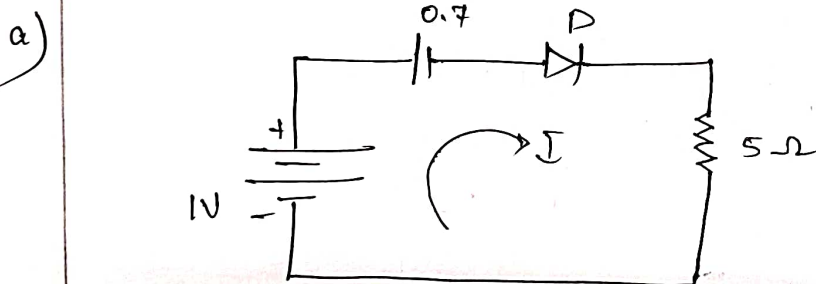- 7) Find the current through the diode assume diode is silicon and forward resistance 0.



$$V_{in} - V_k - V_r = 0$$

∴ KVL law

$$1 - 0.7 - IR = 0$$


$$1 - 0.7 - I \times R = 0$$

$$1 - 0.7 - I \times 5 = 0$$

$$I = \frac{1 - 0.7}{5} = \frac{0.3}{5} = 0.06A = 60 \times 10^{-3}A$$

$$\therefore I = 60 \text{ mA}$$

c)

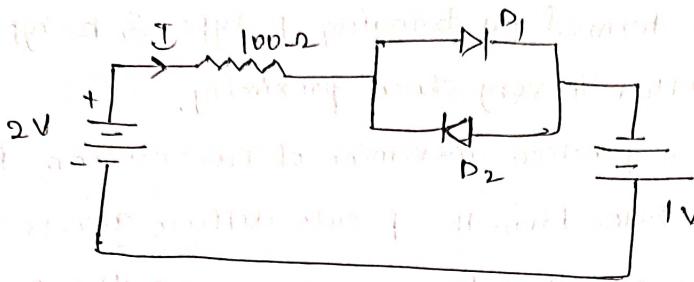

$$V_{in} - I R - V_k + V_{in} = 0 \quad \text{--- (1)}$$

$$V_{in} - I R - V_k + V_{in} \quad \text{--- (2)}$$

$$2 - I_1 R - 0.7 - 1 = 0$$

$$2 - I_2 R + 0.7 + 1$$

$$2 - I_1(100) + 0.3$$

$$2 - I_2(100) + 1.7$$

$$I_1(100) = 0.3 - 2$$

$$I_2 = \frac{3.7}{100}$$

$$I_1 = \frac{2.3}{100}$$

$$I_1 = 0.023 \text{ A} = 23 \times 10^{-3}$$

$$I_2 = 0.037 \text{ A} = 37 \times 10^{-3}$$

$$I_1 = 23 \text{ mA}$$

$$\therefore I_2 = 37 \text{ mA}$$

$\therefore$  current

$$I = I_1 + I_2$$

$$= 23 + 37$$

$$I = 60 \text{ mA}$$

