

Module 2

Assignment - 2.

1] Explain various currents flowing through the BJT transistor.

i) Emitter current:

- Total current flowing into the emitter terminal of BJT.
- It is the sum of base and collector currents in an ideal transistor ($I_E = I_B + I_C$).
- I_E is approx equal to I_C because the base current is small compared to I_C .

ii) Collector current:

- Current flowing through the collector terminal of BJT.
- It is controlled by the base current (I_B) and is typically in the milliampere (mA) range.
- In an NPN transistor, when I_B allows electron flow, a larger I_C flows from the collector to emitter.
- In an PNP transistor, I_C flows from emitter to the collector when I_B allows hole flow.

iii) Base current:

- Current flowing into the base terminal of BJT.
- It controls the transistor's operation and typically is μA range.
- For NPN transistor, I_B allows electron flow from emitter to base.
- For PNP transistor, I_B allows hole flow from the emitter to the base.

2] Explain the transistor biasing circuit with relevant explanation.

• Transistor Biasing: Ensures a transistor operates in the desired region for amplification.


• Fixed Bias circuit:

- Uses resistors to ~~explain~~ set base voltage (V_B).
- Collector voltage (V_C) connects through a resistor (R_C) to supply voltage (V_{CC}).


Self-bias Circuit:

- Relies on the voltage across an emitter resistor (R_e) for base biasing.
- Base voltage (V_b) is determined by R_e and base-emitter voltage (V_{be}).

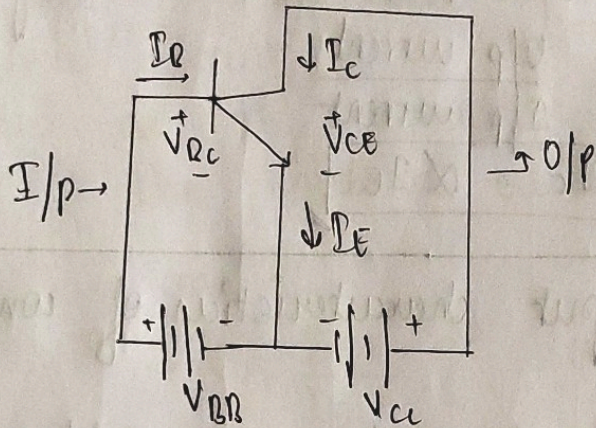
3] Explain input and output characteristics of common emitter configuration.
 → Common-emitter



Input character

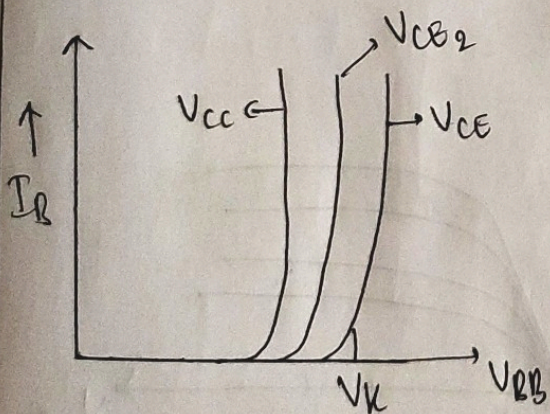

Output character

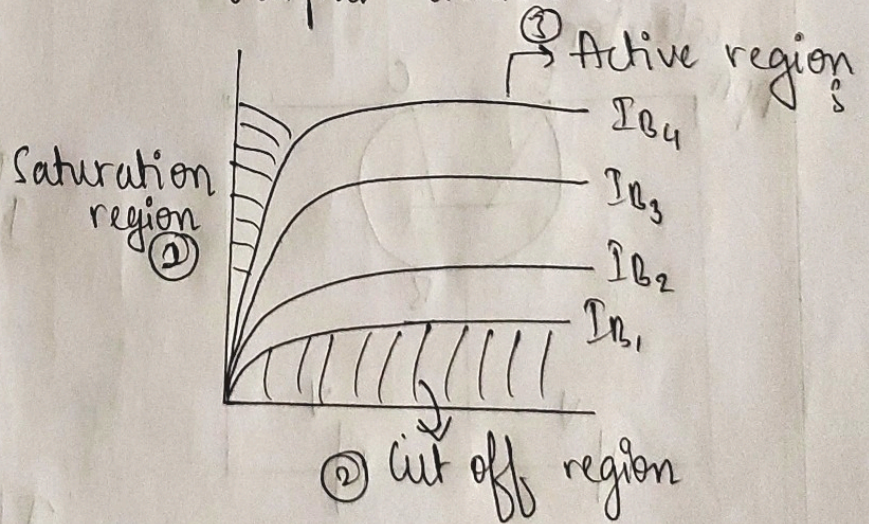

Output characteristics :

It provide 3 different regions:



- Saturation:** In this region base & emitter must be forward bias and collector and emitter also to be forward bias. It gives max collector current (I_C).

2) Cut off: In this region base emitter is in reversed bias and collector and emitter also to be reversed bias. When BE is reversed bias $I_B = 0$. Current gain $= \beta = \frac{\text{Output Current}}{\text{Input Current}}$

3) Active region: In this region base emitter is in forward bias and collector emitter is in reversed bias. In this region transistor is used as amplifier
 $\alpha = \frac{\text{O/p current}}{\text{I/p current}}$
 $I_C = \alpha I_E$

  4) Explain input output characteristics of common base configuration

Common-base: The base is common b/w emitter and collector.



$$I_E = I_B + I_C$$

MA MA MA

$$I_B = 0$$

$$I_E = I_C$$

I/p current = I_E

I/p voltage = V_{EB}

$$\text{O/p} = V_{EC} \ \& \ I_C$$

O/p & I/p values are in phase

In case of common-base configuration the current gain is

$$\alpha = \frac{\text{O/p current}}{\text{I/p current}}$$

$$\alpha = \frac{I_c}{I_E}$$

$$\boxed{I_c = \alpha I_E}$$

$$\alpha = 0.9 \sim 1$$

↓
practical

↳ Theory

5) Define α & β . Determine relationship between α & β .
 α is defined as the ratio of the collector current to the emitter current.

β is defined as the current gain which is given by the ratio of the collector current to base current.

Relation b/w α and β

$$\beta = \frac{I_c}{I_B}$$

$$\alpha = \frac{I_c}{I_E}$$

$$I_E = I_c + I_B$$

$$\alpha = \frac{I_c}{I_E} = \frac{I_c}{I_c + I_B}$$

Divide Numerator & Denominator by I_B

$$= \frac{I_c/I_B}{I_c/I_B + I_B/I_B}$$

$$\boxed{\alpha = \frac{\beta}{1 + \beta}}$$

Similarly

$$\beta = \frac{I_c}{I_B}$$

$$= \frac{I_c/I_E}{I_E/I_c - I_c/I_E}$$


$$\boxed{\beta = \frac{\alpha}{1 - \alpha}}$$

6] Make use of N-channel enhancement type MOSFET and describe the construction & working

MOSFET is different from JFET has no pn junction instead gate is insulated from channel by silicon dioxide (SiO_2)

Enhancement MOSFET

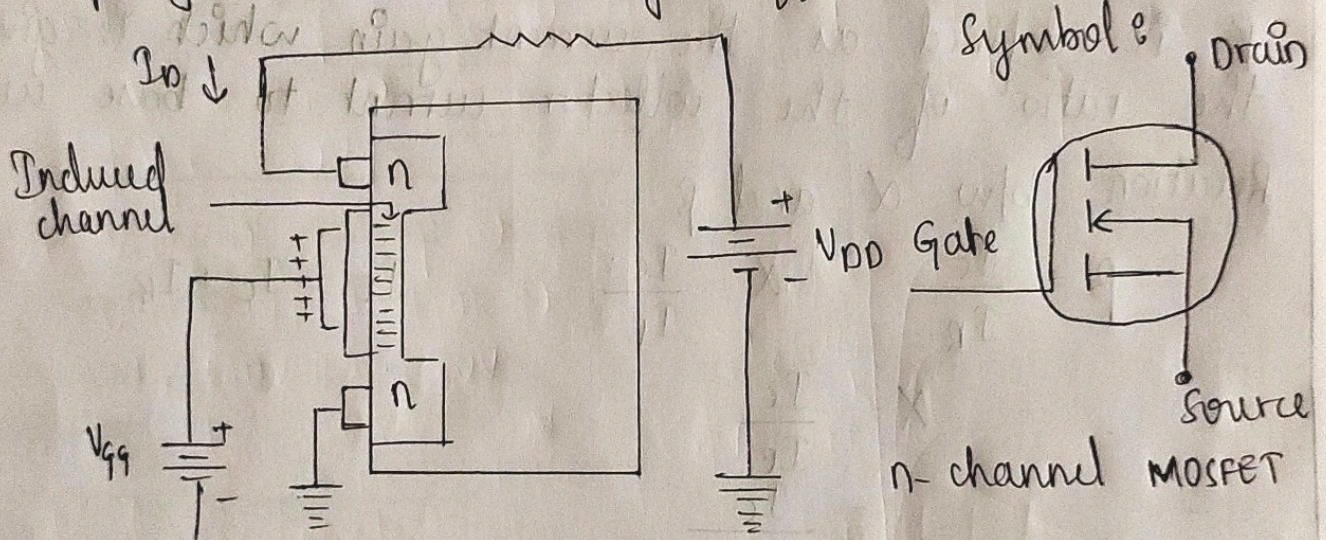- It operates in enhancement mode, has no depletion region
- The construction of n-channel enhancement mode MOSFET is shown below. Here n regions are diffused into p-type substrate using diffusion process.




- For n-channel device, positive gate voltage above threshold voltage induced channel by creating thin layer of negative charges in the substrate region. i.e. adjacent to SiO_2 layer conductivity of this channel is enhanced by increased gate to source voltage and hence it pulls more electrons into the channel
- Gate voltage below threshold no channel created

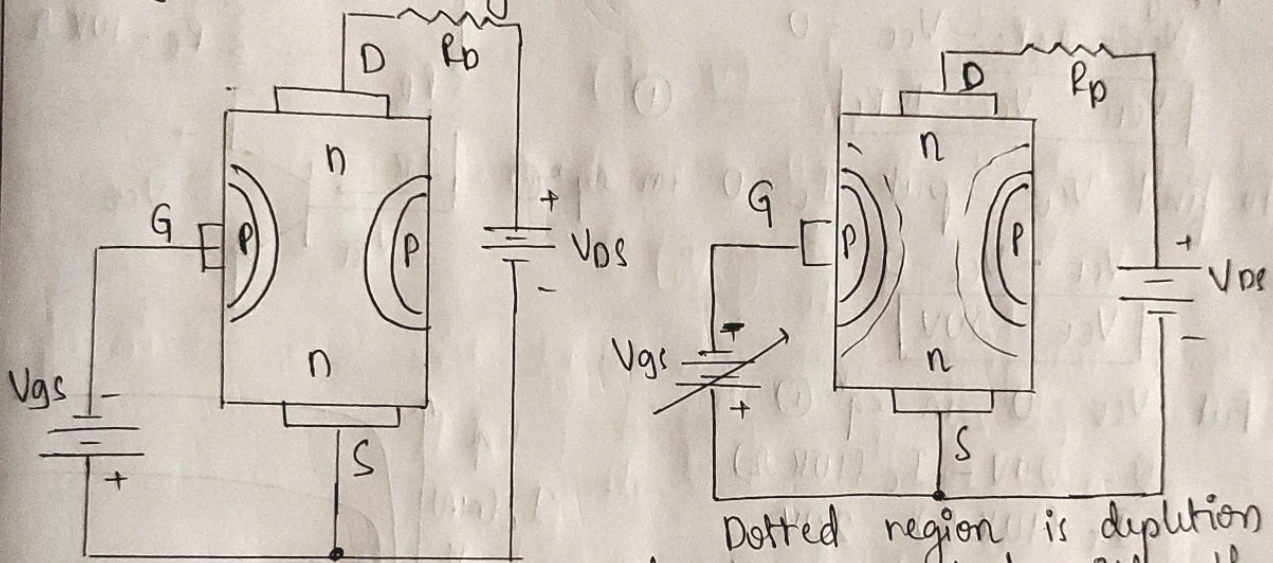7) Make use of n-channel JFET to describe its operation & characteristics.

Operation:

To illustrate operation of JFET, the fig below shows dc bias voltage applied to an n-channel device. V_{DS} provides a drain to source voltage and supplies current from drain to source. V_{GS} set reverse bias voltage between gate & source.



Dotted region is depletion region

Case a: The JFET is always operated with the gate to source junction reverse biased. The reverse biasing of G-S with negative voltage produces a depletion region along pn-junction, and extend in n-channel. Hence, increase in resistance by restricting channel.

Case b: As voltage across gate & source increases, depletion region created by reverse bias increases and narrow the channel which increases the resistance of the channel and decreases I_D .

* NOTE: Distance b/w dotted lines decreases.
Case c: As voltage across V_{GS} decreases, depletion region created by reverse bias decreases and widens the channel (which decreases the resistance of the channel and increase I_D).
 * NOTE: Distance b/w dotted lines increases.

Characteristics:

- Voltage-controlled
- High input Impedance
- Low Noise
- Temperature sensitive

8] Draw the DC load line for circuit shown.

$$V_{CC} = +20V$$

→ Apply KVL to collector-emitter,

$$V_{CC} - I_C R_C - V_{CE} = 0$$

$$\boxed{V_{CE} = V_{CC} - I_C R_C} \quad \text{--- (1)}$$

To find V_{CE} , put $I_C = 0$ in eqⁿ (1)

$$V_{CE} = V_{CC} - 0$$

$$\boxed{V_{CE} = 20V}$$

Put $V_{CE} = 0$ in eqⁿ (1)

$$0 = 20V - I_C (10k\Omega)$$



$$I_C (10k\Omega) = 20V$$

$$I_C = \frac{V_{CC}}{R_C} = \frac{20V}{10k\Omega} = 2mA$$

DC load line points:

$$1) I_C = 0, V_{CE} = 20V$$

$$2) V_{CE} = 0, I_C = 2mA$$

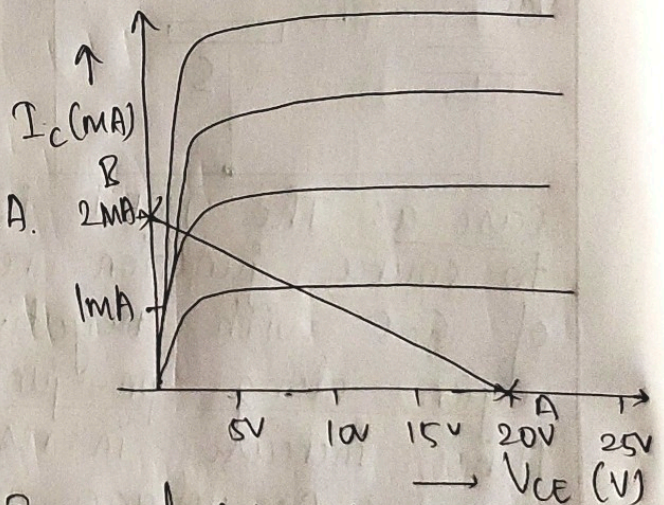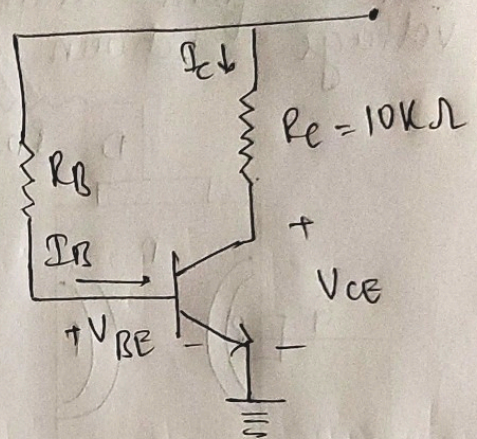

9] Calculate the values of I_C , I_E and β_{dc} for a transistor with $\alpha_{dc} = 0.98$ and $I_B = 100\mu A$.

$$\beta_{dc} = \frac{\alpha_{dc}}{1 - \alpha_{dc}} = \frac{0.98}{1 - 0.98} = 49$$

$$I_E = \beta_{dc} I_B = 49 \times 100 = 4900\mu A$$

Module 3

10) Briefly discuss ideal characteristics of Op Amp.

→ i) Common mode rejection ratio -

It is ratio of differential mode gain to the common mode gain.

$$\text{i.e. CMRR} = \frac{A_{DM}}{A_{CM}}$$

2) Output offset voltage - The actual o/p when i/p of op amp is zero is called output offset voltage.

3) Input offset voltage - Because of unavoidable imbalance inside the op amp a small voltage is been applied b/w the i/p terminals that make o/p is zero.

4) I/p resistance - It is measured b/w inverting & non-inverting terminal due to this it will not allow to draw current from voltage source (∞ ideally).

5) O/p resistance - The resistance is measured b/w the o/p terminal of op amp & ground (0 ideally).

6) Slew rate - It is defined as how fast the o/p of op amp can change to the change in i/p i.e. the max rate at which the o/p can change.

7) Open loop & closed loop configuration -

• In case of open loop the o/p is directly proportional to i/p with some proportionality constant.

• In case of closed loop the feedback structure is existing & this will control the system. It provides stablised system with less gain factor.

11) Derive an expression for integrator.
→ A circuit in which the o/p voltage waveform is the integral of i/p voltage waveform is called Integrator.

KCL at node ② ie V_2 ,

$$i_1 = i_R + i_f \quad \text{--- (1)}$$

since I_R is small,

$$I_1 \approx I_f \quad \text{--- (2)}$$

The current through capacitor is,

$$i_c = C_f \frac{dV_c}{dt} \quad \text{--- (3)}$$

$$\frac{V_{in} - V_2}{R_1} = C_f \frac{d}{dt} (V_2 - V_o)$$

W.K.T $V_1 = V_2 \approx 0$ because A is very large.


$$\therefore \frac{V_{in}}{R_1} = C_f \frac{d}{dt} (-V_o)$$

Now integrate both side w.r.t time to obtain o/p voltage

$$\int_0^t \frac{V_{in}}{R_1} dt = \int_0^t C_f \frac{d}{dt} (-V_o) dt$$

$$\frac{1}{R_1} \int_0^t V_{in} dt = -C_f \int_0^t \frac{d}{dt} (V_o) dt$$
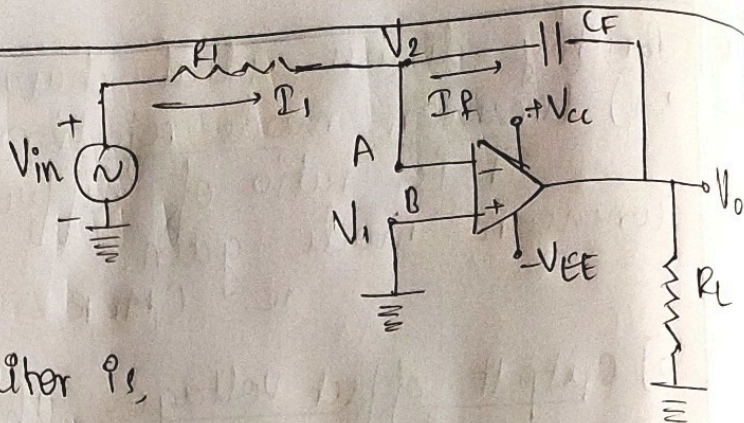
$$V_o = -\frac{1}{R_1 C_f} \int_0^t V_{in} dt + C$$



12] Devise an expression for 3 input summing circuit.

$$I = I_1 + I_2 + I_3$$

$$I = I' + I_f$$


$$I = I_f$$

$$I_f = (I_1 + I_2 + I_3)$$

$$\text{Let } R_1 = R_2 = R_3 = R_f$$

$$V_B - V_f - V_o = 0$$

$$V_B - V_o = I_f R_f$$

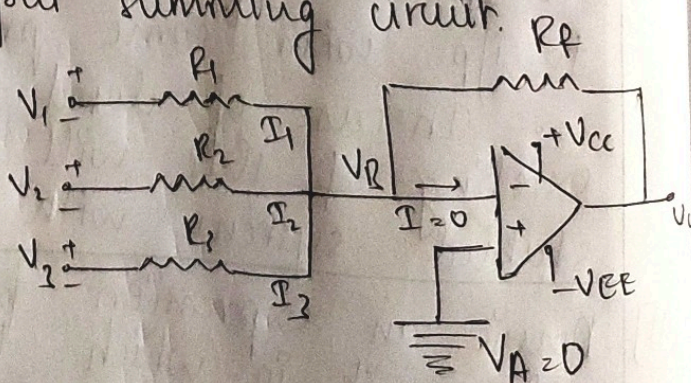

$$\frac{-V_o}{R_f} = I_f \quad I_1 = \frac{V_1 - V_R}{R_1} \quad I_2 = \frac{V_2 - V_R}{R_2}$$

$$\frac{-V_o}{R_f} = I_1 + I_2 + I_f$$

$$\frac{-V_o}{R_f} = \frac{+V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3}$$


$$-V_o = V_1 + V_2 + V_3$$

$$V_o = -(V_1 + V_2 + V_3)$$

$$(R_1 = R_2 = R_3 = R_f)$$

13] Explain with a neat block diagram of an Op-Amp.
 An operational amplifier is a direct coupled high-gain amplifier used to amplify AC and DC signals.

Block diagram :-

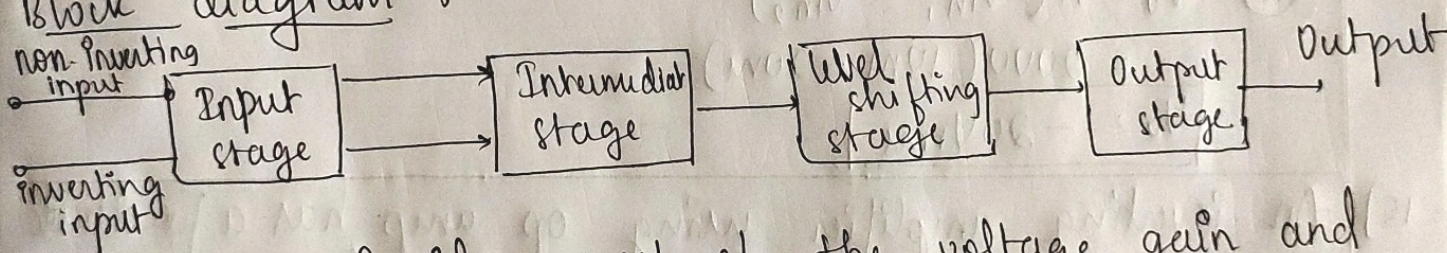


- * Input stage: Provides most of the voltage gain and establishes input resistance
- * Intermediate stage:
 - driven by the output of first stage
 - o/p level of intermediate stage is above ground as direct coupling is used
- * Level stage:
 - level shifting stage is used to shift the o/p of intermediate stage downward.
- * Output stage:
 - increases the o/p voltage swing
 - raises the current supplying capability
 - provides low o/p resistance

14) Determine the o/p voltage in each of the following cases for the open-loop differential amplifier.

a) $V_{in_1} = 5 \text{ V dc}$, $V_{in_2} = -7 \text{ V dc}$

 b) $V_{in_1} = 10 \text{ mV}$, $V_{in_2} = 20 \text{ mV}$



(a) W.K.T $V_o = A (V_{in_1} - V_{in_2})$
 $= 2000 (5 - (-7))$
 $V_o = 2400 \text{ V}$

(b) $V_o = A (V_{in_1} - V_{in_2})$
 $= 2000 (10 \text{ m} - 20 \text{ m})$
 $V_o = -20 \text{ Vrms}$

15) An inverting amplifier using op-amp has a feedback resistor of 10 k . Calculate the gain of op-amp & o/p voltage if it supplied with an input 0.5 V .

Given, $R_f = 10 \text{ k}\Omega$, $R_1 = 1 \text{ k}\Omega$, $A = ?$, $V_o = ?$, $V_{in} = 0.5 \text{ V}$

$A_v = -\frac{R_f}{R_1} = \frac{-10 \text{ k}}{1 \text{ k}}$

$A_v = -10$

Inverting amplifier

$V_o = -A \cdot V_{in}$

$A_v = \frac{R_f}{R_1}$


$V_o = -\frac{R_f}{R_1} V_{in}$

$V_o = \frac{-10 \text{ k}}{1 \text{ k}} \cdot 0.5$

$V_o = -5 \text{ V}$

16] Derive voltage gain for inverting amplifier

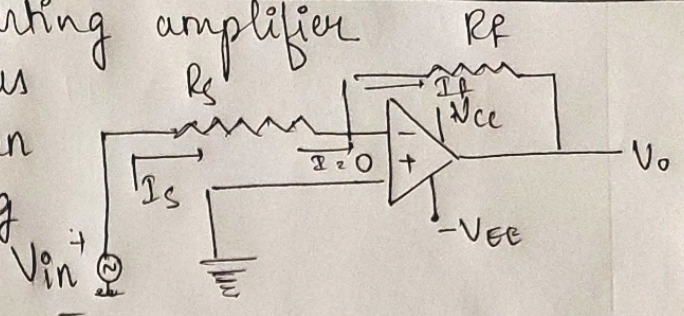→ An amplifier which produces a phase shift of 180° between i/p & o/p is called inverting amplifier



In this circuit,

$$I_s = I + I_f$$

$$\boxed{I_s = I_f} \quad \text{--- (1) As } I_i = 0$$

$$V_1 = \text{Ground} = 0$$

$$V_1 = V_2 = 0$$

$$V_1 - V_2 = V_d$$

W.K.T. $I = \frac{V_1 - V_2}{R}$

W.K.T. $I_s = \frac{V_{in} - V_2}{R_s} \quad \text{--- (2)}$

$I_f = \frac{V_2 - V_o}{R_f} \quad \text{--- (3)}$

Put (2) & (3) in eqⁿ (1)

$$I_s = \frac{V_{in}}{R_s} \quad I_f = \frac{-V_o}{R_f}$$

$$I_s = I_f$$

$$\frac{V_{in}}{R_s} = \frac{-V_o}{R_f}$$

$$\boxed{V_o = -\frac{R_f}{R_s} \cdot V_{in}}$$

Here, Gain = $A = \frac{R_f}{R_s}$

$$\therefore \boxed{V_o = -A \cdot V_{in}}$$