

3) Efficiency: - (2)

$$\text{Efficiency} = \frac{\text{input power}}{\text{output power}} = \frac{P_{AC}}{P_{DC}}$$

$$\eta = \frac{P_{OIP}}{P_{DC}} = \frac{P_{deac}}{P_{DC}} = \frac{V_{dc} I_{dc}}{V_{rms} I_{rms}}$$

3) Efficiency: - (2)

$$\text{Efficiency} = \frac{\text{output power}}{\text{input power}} = \frac{P_{DC}}{P_{AC}}$$

$$\eta = \frac{P_{OIP}}{P_{DC}} = \frac{P_{deac}}{P_{DC}} = \frac{V_{dc} I_{dc}}{V_{rms} I_{rms}}$$

$$V_{dc} = I_{dc} \cdot R_L \quad \underline{P_{DC}} \quad I_{dc} = \frac{V_{dc}}{R_L}, \quad V_{rms} = I_{rms} (r_f + R_L)$$

$$\eta = \frac{I_{dc}^2 \cdot R_L}{I_{rms}^2 (r_f + R_L)}$$

$$I_{dc} = I_m / \pi$$

$$I_{rms} = I_m / 2$$

$$\eta = \frac{I_m^2 / \pi^2 \cdot R_L}{I_m^2 / 4 (r_f + R_L)}$$

$$= \frac{4 \times R_L}{\pi^2 (r_f + R_L)}$$

$$\eta = \frac{4}{\pi^2} = 0.405 \times 100 \%$$

$$\boxed{\eta = 40.5\%}$$

The efficiency is very much less in HWR hence to increase the efficiency we should use more than 1 diode i.e. FWR.

* Peak inverse voltage (PIV) it is the reverse voltage when diode is non conducting. In HWR, $PIV = V$