


21/5/24

## Operational Amplifier


SONA ROOPA Page No.

Date

## \* Block diagram

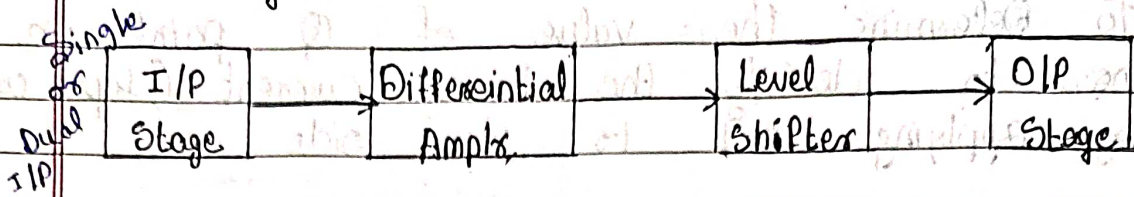


## \* Differential Amplifier [DA]

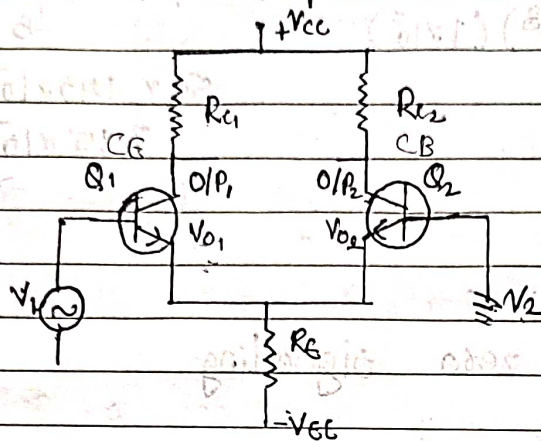

- Contains two transistors which alternately acts as CB and CE. The I/P signal goes to CE and become out of phase that out of phase signal goes to CB and the final output is in phase with the Input signal.
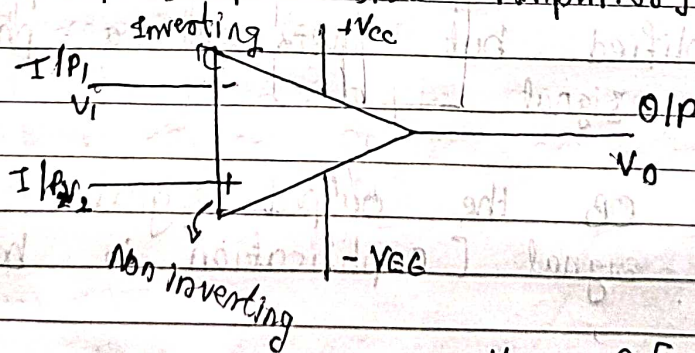
## \* Op. Amp [Operational Amplifier] symbol




$$V_0 = A[V_2 - V_1]$$

where  $A$  is the gain [voltage gain]
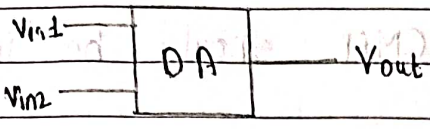
## \* Differential mode and common mode signals

- Differential Amplifier :- It is taking two different signals and the difference of those two signals are amplified is called differential amplifier.



$$V_{out} = A_v V_{in}$$

$$V_{in} = V_{in1} - V_{in2}$$


$$V_{out} = A_v [V_{in1} - V_{in2}]$$

In common mode the differential amplifiers will take two input signals and those two input signals are in phase.

$$V_1 = V_2$$

In case of differential mode the two input signals to the differential amplifiers are out of phase (180°)

$$V_1 = -V_2$$

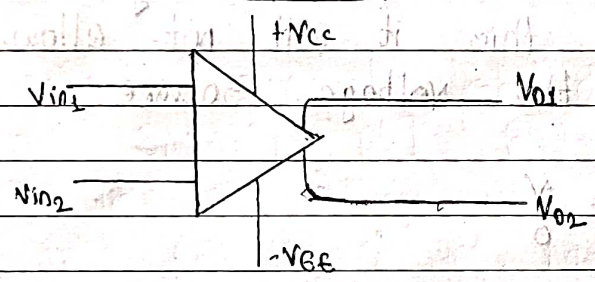

$$V_{in1} = A_v, V_{in2} = \text{Grounded}, V_{out1} = A_v, V_{out2} = A_v$$

In case of common mode the chance of getting O/P is zero volt.

In case of differential mode the output is two times of i.e. I/P

\* Parameters of OP. AMP

Common mode rejection ratio :-  
It is the ratio of differential gain to the common mode gain i.e.  $CMRR = \frac{A_{DM}}{A_{CM}}$

A = gain, DM = Diff mode, CM = common mode

- It will be better when CMRR should be infinite.  
∴  $(A_{CM} = 0)$

- O/P Offset voltage :- <sup>voltage</sup>  
The actual O/P when the input of OP.AMP is zero is called O/P offset voltage.

- I/P Offset voltage :-  
Because of the unavoidable imbalance inside the OP.AMP a small voltage is being applied b/w the two input terminals that makes output zero.

- I/P resistance :-  
It is measured b/w inverting and non inverting terminal. due to this it will not allow the current to draw from the voltage source.

$$I = 0$$

$$R = \frac{V}{0}$$

$R = \infty \rightarrow$  ideally.

- O/P resistance :-  
This resistance is measured b/w the output terminal of an OP.AMP and the ground.  
∴  $R_{OP} = 0$  [ideally]


- Slew rate :-  
It is defined as how fast the output of an OP.AMP can change to the change in input i.e. the maximum rate at which the output can change.

- Op.


Open loop and closed loop configuration:

In case of open loop system the output is directly proportional to input with some proportionality const [Open loop gain]. In this case the system is unstable and gain is very high.

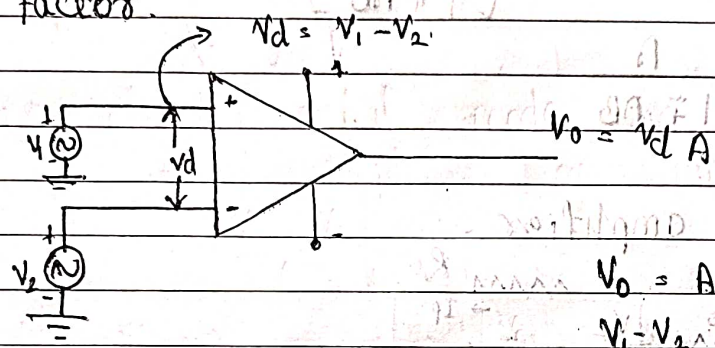In case of closed loop system the feedback structure is existing and this will control the system it provides stabled system with less gain factor.



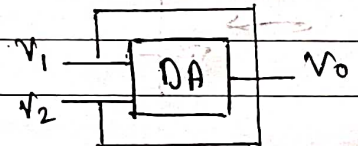$V_o = A [V_1 - V_2]$   
 $V_1 - V_2 = 2V$



Open loop


Gain =  $A = 10$ ,  $B = 0.1$

Positive Gain =  $\frac{A}{1 + AB}$

closed Gain +ve =  $\infty$   
with +ve feedback

closed Gain -ve =  $5$   
with -ve feedback

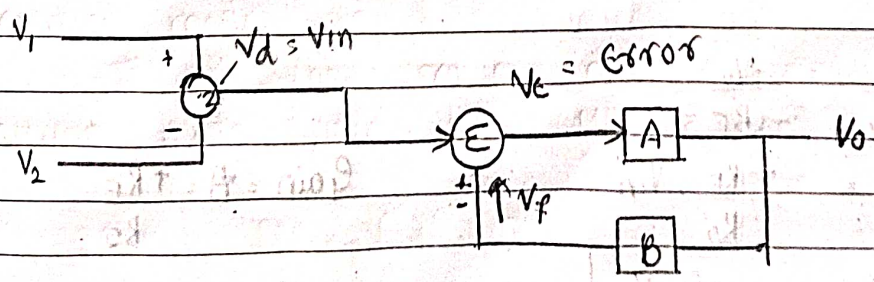\* +ve feedback system is uncontrollable / unstable  
\* -ve feedback system is controlled / stable



$$V_B = V_B A \quad \text{--- (1)}$$

$$V_F = V_O B \quad \text{--- (2)}$$

$$V_B = V_{in} + V_F$$

$$V_O = V_B A$$

$$= (V_{in} + V_F) A$$

$$= V_{in} A + A V_O B$$


$$V_O - V_O A B = V_{in} A$$

$$V_O [1 - A B] = V_{in} A$$

$$V_O = V_{in} \left[ \frac{A}{1 - A B} \right]$$

$$\text{Gain} = \frac{A}{1 - A B}$$

**Inverting amplifier**

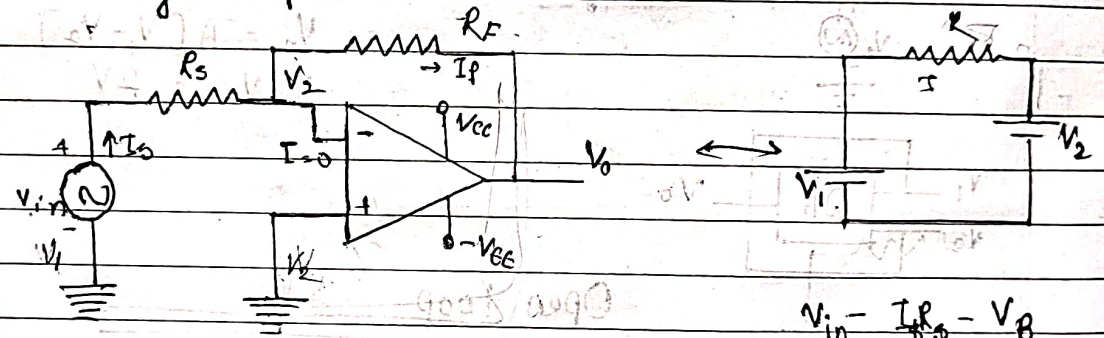

$$I_S = I + I_F \quad V_1 = \text{Ground} = V_2$$

$$I_S = I_F \quad V_1 = V_2 = 0$$

$$I_S = \frac{V_{in} - V_2}{R_s}$$

$$I_F = \frac{V_2 - V_o}{R_f}$$

$$V_{in} - I_S R_s - V_B$$

$$I_S = \frac{V_{in} - V_B}{R_s}$$

$$V_2 - I_F R_f - V_o = 0$$

$$V_B - I_F R_f - V_o = 0$$

$$V_B - V_o = I_F R_f$$

$$I_F = \frac{V_B - V_o}{R_f}$$

$$I_S = \frac{+V_{in}}{R_s} \quad I_F = \frac{-V_o}{R_f}$$


$$\frac{V_{in}}{R_s} = \frac{-V_o}{R_f}$$

$$V_o = \frac{-R_f}{R_s} V_{in}$$

$$\text{Gain} = A = \frac{-R_f}{R_s}$$

$$V_o = -A \cdot V_{in}$$

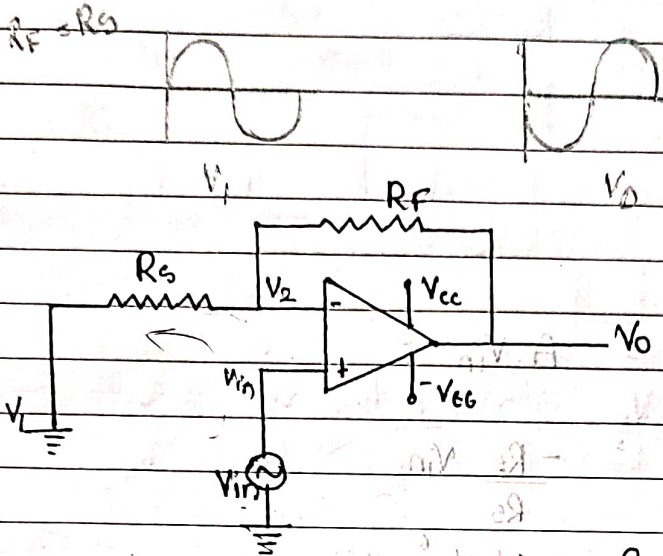- i)  $R_F > R_S$   $A \uparrow$ ,  $V_o \downarrow$  → Amplified but out of phase.
- ii)  $R_F < R_S$   $A \downarrow$ ,  $V_o \downarrow$  -
- iii)  $R_F = R_S$   $A = \text{const}$   $V_o \neq V_i$  but inverted



$V_{EA} = \text{Grounded}$   
 $V_1 = V_2$

$$V_1 - V_{in} = R_S I_S$$

$$I_S = \frac{V_1 - V_{in}}{R_S} = \frac{-V_{in}}{R_S}$$

$$I_S = I_F$$

$$\frac{-V_{in}}{R_S} = \frac{-V_o + V_{in}}{R_F}$$

$$-V_o = \frac{R_F}{R_S} V_{in} - V_{in}$$

$$-V_o = \frac{R_F}{R_S} V_{in} - \frac{R_F}{R_S} V_{in} + V_{in}$$

$$-V_o = \frac{R_F}{R_S} V_{in} - \frac{R_F}{R_S} V_{in} + V_{in}$$

$$-V_o = \frac{R_F}{R_S} V_{in} - \frac{R_F}{R_S} V_{in} + V_{in}$$

$$V_o = \frac{R_F}{R_S} V_{in}$$

$$\frac{-V_{in}}{R_S} + \frac{V_{in}}{R_F} = \frac{V_o}{R_F}$$

$$V_o = R_F V_{in} \left[ \frac{1}{R_S} + \frac{1}{R_F} \right]$$


$$V_o = V_{in} \left[ \frac{R_F}{R_S} + \frac{R_F}{R_F} \right]$$

$$V_o = V_{in} \left[ 1 + \frac{R_F}{R_S} \right]$$

① For Inverting Amplifier Determine closed loop gain if  $R_f = 1M\Omega$  &  $R_s = 20k\Omega$  Also find  $V_{in}$  &  $V_o = 2V$

② For non Inverting Amplifier find  $V_o$  if  $V_{in} = 3V$  &  $V_{in} = 0.2V$   $R_f = 360k\Omega$  &  $R_s = 120k\Omega$

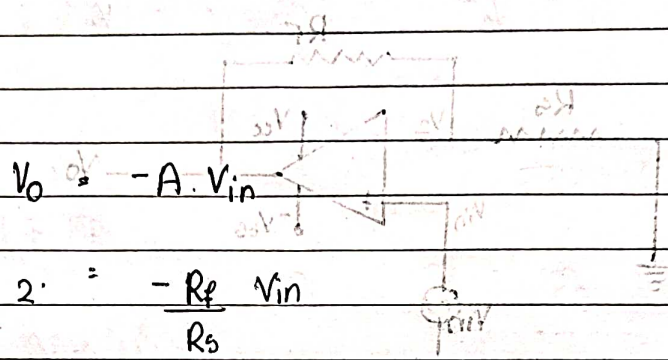③  $R_f = 1 \times 10^6 \Omega$   
 $R_s = 20 \times 10^3 \Omega$   
 $V_o = 2V$   
 $V_{in} = ?$



$$V_o = -A \cdot V_{in}$$

$$2 = -\frac{R_f}{R_s} V_{in}$$

$$-2 \times 10^4 = -1 \times 10^6 \cdot V_{in}$$

$$\frac{-2 \times 10^4}{-1 \times 10^6} = V_{in}$$

$$-4 \times 10^{-2} V = V_{in}$$

② (i)  $V_{in} = 3V$   
 $R_f = 360 \times 10^3$   
 $R_s = 120 \times 10^3$   
 $V_o = ?$

$$V_o = V_{in} \left[ 1 + \frac{R_f}{R_s} \right]$$

$$= 3 \left[ 1 + \frac{360 \times 10^3}{120 \times 10^3} \right]$$

$$V_o = 12V$$


when  $V_{in} = 0.2V$

$$V_o = 0.2 \left[ 1 + \frac{360 \times 10^3}{120 \times 10^3} \right]$$

$$V_o = 0.8V$$

\* OP AMP as a SUMMER

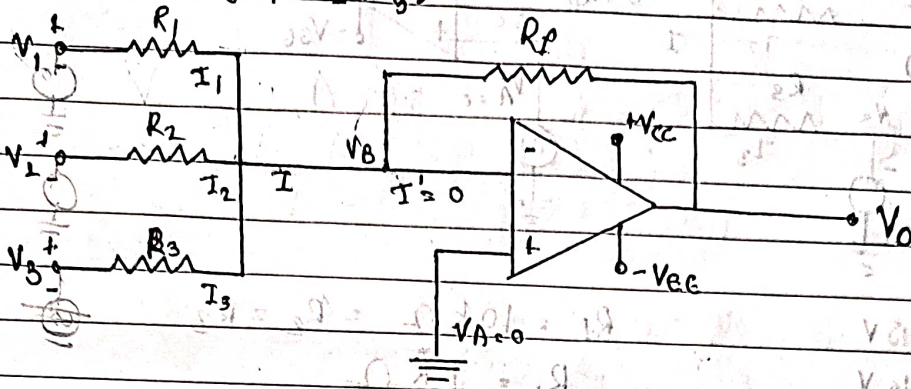Three input signals to inverting  
 $V_o = - (V_1 + V_2 + V_3)$



$$I = I_1 + I_2 + I_3$$

$$R_1 = R_2 = R_3 = R_f$$

$$I = I' + I_f$$

$$I = I_f$$

$$I_f = (I_1 + I_2 + I_3)$$

$$V_B - V_P = -V_o = 0$$

$$V_B - V_o = I_f R_f$$

$$\frac{-V_o}{R_f} = I_f$$


$$\frac{-V_o}{R_f} = I_1 + I_2 + I_3$$

$$\frac{-V_o}{R_f} = \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3}$$

$$-V_o = V_1 + V_2 + V_3 \quad (R_1 = R_2 = R_3 = R_f)$$

$$V_o = - (V_1 + V_2 + V_3)$$

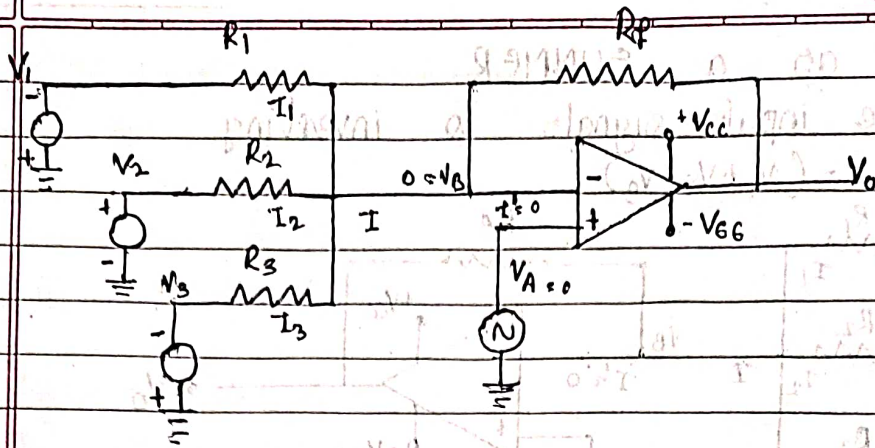Q Let  $V_1 = -5V$ ,  $V_2 = 10V$ ,  $V_3 = -12V$ . Draw the SUMMER circuit with inverting configuration and determine  $V_o$ . If  $R_f = 10k\Omega$ ,  $R_2$  &  $R_3 = 10k\Omega$ ,  $R_1 = 1k\Omega$



$V_1 = -5V$

$V_2 = 10V$

$V_3 = -12V$

$V_0 = ?$

$R_f = 10k\Omega = R_2 = R_3$

$R_1 = 1k\Omega$

$$\frac{-V_0}{R_f} = \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3}$$

$$\frac{-V_0}{1 \times 10^4} = \frac{-5}{1 \times 10^3} + \frac{10}{1 \times 10^4} - \frac{12}{1 \times 10^4}$$

$$\frac{-V_0}{1 \times 10^4} = \frac{-5}{1 \times 10^3} - \frac{2}{1 \times 10^4}$$

$$= -5 \times 10^{-3} - 2 \times 10^{-4}$$


$$\frac{-V_0}{1 \times 10^4} = -5.2 \times 10^{-3}$$


$$\therefore V_0 = +5.2 \times 10^{-3} \times 1 \times 10^4$$

$$V_0 = 52V$$

Q Design the summer circuit with  $R_f = 10k\Omega$  to obtain the O/P  $V_0 = -(0.1V_1 + V_2 + 10V_3)$

Subtractor :

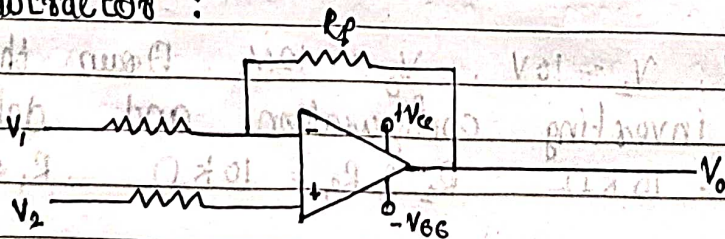

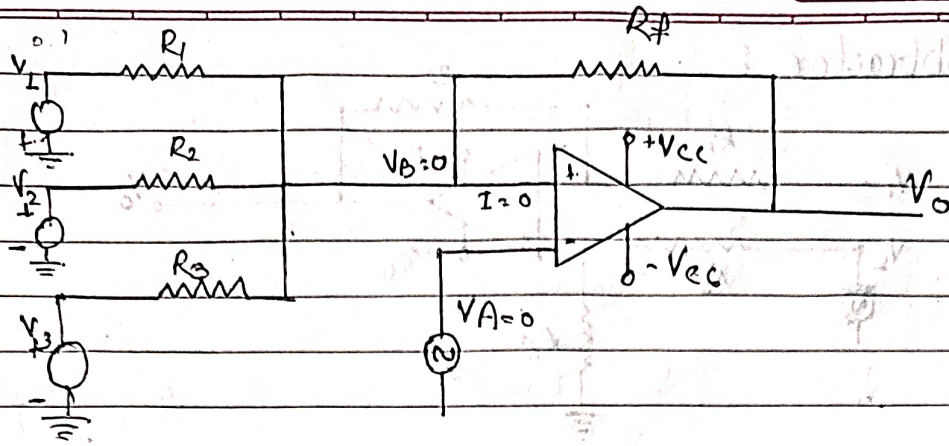

$$-V_0 = \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3}$$

$$\frac{-V_0}{10 \times 10^3} =$$

$$\frac{-(0.1V_1 + V_2 + 10V_3)}{10 \times 10^3} = \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3}$$

$$-0.1V_1 - V_2 - 10V_3 = 10 \times 10^3 \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right)$$

$$-0.1V_1 - V_2 - 10V_3 = \frac{R_f V_1}{R_1} + \frac{R_f V_2}{R_2} + \frac{R_f V_3}{R_3}$$

$$\frac{R_f}{R_1} = 0.1 \quad \frac{R_f}{R_2} = 1 \quad \frac{R_f}{R_3} = 10$$

$$\frac{10 \times 10^3}{R_1} = 0.1$$

$$\frac{10 \times 10^3}{R_2} = 1$$

$$\frac{10 \times 10^3}{R_3} = 10$$

$$R_1 = 100 \text{ k}\Omega$$

$$R_2 = 10 \text{ k}\Omega$$

$$R_3 = 1 \text{ k}\Omega$$


$$-V_0 = R_f \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right)$$

$$10 \times 10^3 \left( \frac{10 V_1}{100 \times 10^3} + \frac{10 V_2}{10 \times 10^3} + \frac{10 V_3}{1 \times 10^3} \right)$$


$$= \left( \frac{10 V_1}{100} + \frac{10 V_2}{10} + \frac{10 V_3}{1} \right)$$

$$V_0 = -(0.1V_1 + V_2 + 10V_3)$$

\* Subtractor :

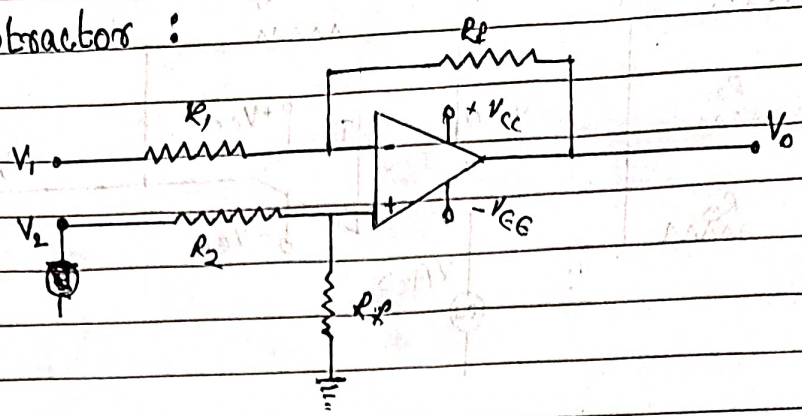


Let assume  $V_2 = 0$

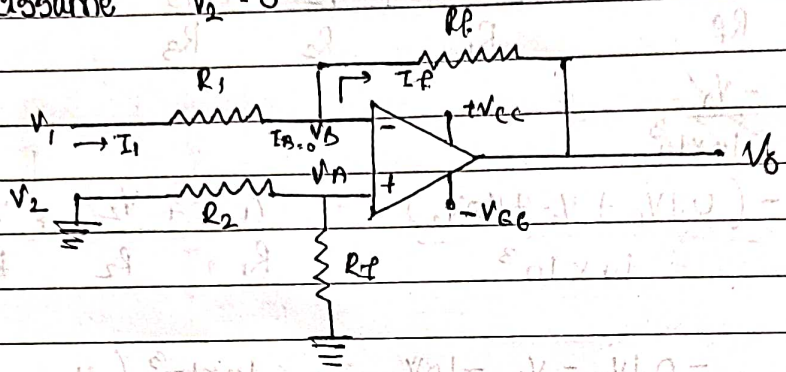

Since the voltage  $V_A = 0$  due to  $V_2 = 0$  the circuit look like inverting amplifier hence the relation between  $V_0$  w.r to  $V_1$  is

$$V_0 = -\frac{R_f}{R_1} V_{1A} \quad \text{--- (1)}$$

Let assume  $V_1 = 0$

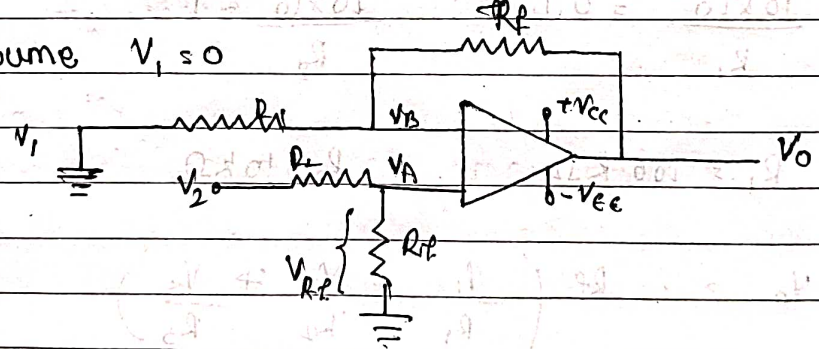

Since  $R_2$  and  $R_f$  are connected in series the current through  $R_2$  is same as current through  $R_f$  hence

$$V_{Rf} = I \cdot R_f$$

$$I = \frac{V_2}{R_2 + R_f} = \frac{V_2 R_f}{R_2 + R_f}$$

$$V_0 = V_{Rf} \left[ 1 + \frac{R_f}{R_1} \right]$$

$$V_o = V_{BP} \left[ 1 + \frac{V_2 R_f}{R_1 (R_2 + R_f)} \right]$$

$$V_o = \frac{V_2 R_f}{R_2 + R_f} \left[ 1 + \frac{R_f}{R_1} \right]$$

$$= \frac{V_2 R_f}{R_2 + R_f} \left[ \frac{R_1 + R_f}{R_1} \right]$$

Assume  $R_1 = R_2 = R$

$$= \frac{V_2 R_f}{R + R_f} \left[ \frac{R + R_f}{R} \right]$$

$$V_o = \frac{V_2 R_f}{R} \quad \text{--- (2)}$$

$$V_{o2} = \frac{V_2 R_f}{R} \quad \text{--- (2)}$$

$$\boxed{V_{o1} = -\frac{R_f}{R} V_1} \quad \text{--- (1)}$$

$$V_o = V_{o1} + V_{o2}$$

$$= \frac{V_2 R_f}{R} - \frac{R_f}{R} V_1$$


$$\boxed{V_o = -\frac{R_f}{R} [V_2 - V_1]}$$

If  $A = 1$

$$V_o = V_2 - V_1$$

\* Open loop and Closed loop

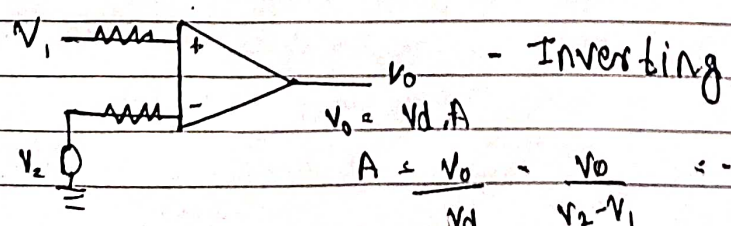- Both loops [ Open & Closed ] are considering 3 configura-tion namely inverting, noninverting and differential




$$V_o = V_d A$$

$$A = \frac{V_o}{V_d} = \frac{V_o}{V_2 - V_1} = -\frac{V_o}{V_1} \quad [V_2 = 0]$$

$$\boxed{V_o = -A V_1}$$

Non-inverting


②

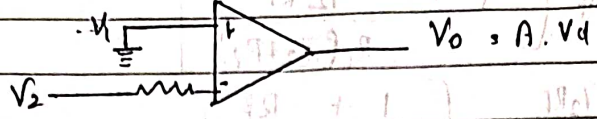

$$A = \frac{V_o}{V_d} \Rightarrow \frac{V_o}{V_2} \quad (V_1 = 0)$$

$$V_o = AV_2$$

③

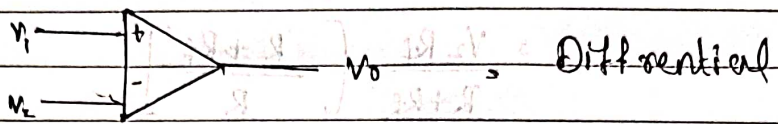


$$V_d = V_2 - V_1$$

$$A = \frac{V_o}{V_d}$$

$$V_o = A.V_d$$

$$V_o = A(V_2 - V_1)$$

\* Voltage follower :

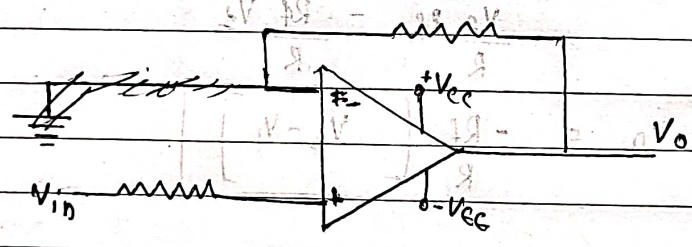

$$V_{in} = V_o$$

No phase difference, no amplification.